
LM3447: Performance Analysis (43 EVM Production Samples)

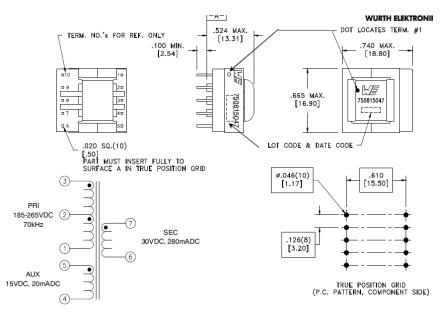Lighting Power Products Longmont Design Center



Design Example: LM3447-A19-230VEVM (Online: http://www.ti.com/tool/Im3447-a19-230vevm)






TI Information – Selective Disclosure

	Тур	Units
Input Voltage	230	V_{RMS}
Output Voltage	30	V
LED Current	275	mA
Output Power	8.25	W
Input Power	10.1	W
Efficiency	82	%
Power Factor	0.95	

- EVM production lot = 150
- Sampled size = 43
- Random sampling
- LM3447MT Tape & Reel
- Xfmr 750815047
 Wurth Electronics China



Schematic: LM3447-A19-230VEVM

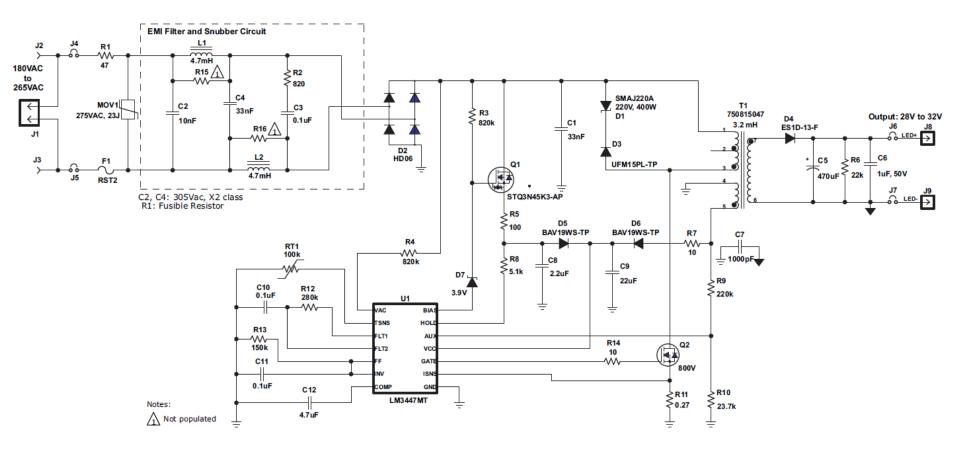



LM3447: Theoretical Analysis (1)

$$P_{IN} = \frac{\pi}{4} \frac{G_{FF}^2 V_{REF}^2}{L_M f_S} \left(\frac{R_{AC}}{R_{FF}}\right)^2$$


- P_{IN} Input power
- L_M Primary side magnetizing inductance
- *f*_s Switching frequency
- G_{FF} Internal gain
- V_{REF} Internal reference
- R_{AC} AC sense resistor (R4)
- R_{FF} Feedforward resistor (R13)

- Input power is function of external components
- Impact of magnetizing inductance: L_M
 - Inversely proportionality
 - Manufacturing spec < ±10%</p>
 - Based on air-gap tolerance (independent of Ferrite material)
- External resistors (ratio)

 R_{AC} & R_{FF} with ±1% tolerance
- Internal IC parameters trimmed and tested to industry standards




Input Power Variation (Production Run)

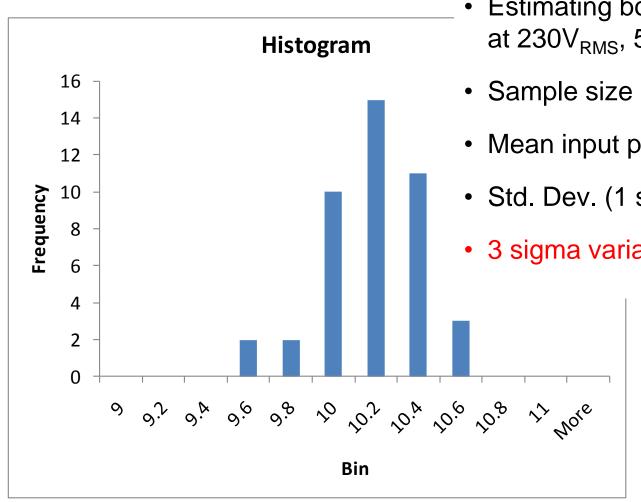

- Estimating board-to-board variations • at 230 V_{RMS} , 50Hz operating point
- Sample size = 43 boards
- Mean input power = 10.1W
- Std. Dev. (1 sigma) = 221mW
- 3 sigma variation= ±6.6%




LED Current Variation

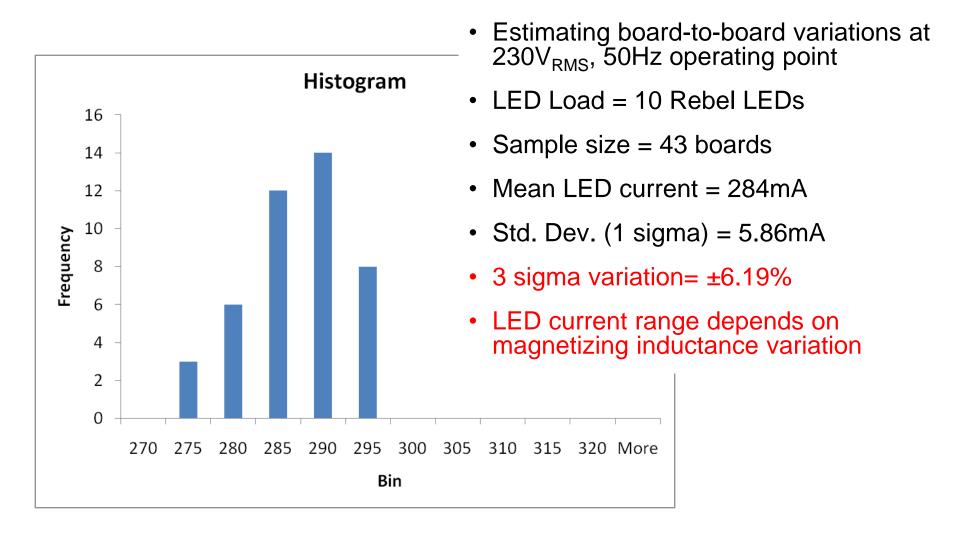



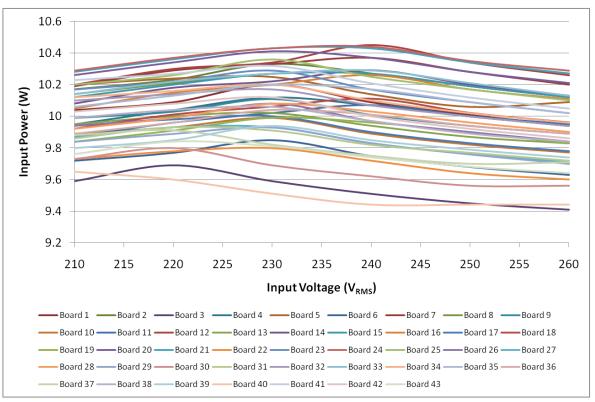Input Power vs. Input Voltage (210V to 260V)




- Input power range for sample size of 43 boards ($210V_{RMS}$ to $260V_{RMS}$)
 - Min = 9.44W (-5.7%)
 - Max = 10.45W (+4.4%)
 - Average = 10.01W

Input power deviation at any given voltage < ±7.5% (3 sigma)




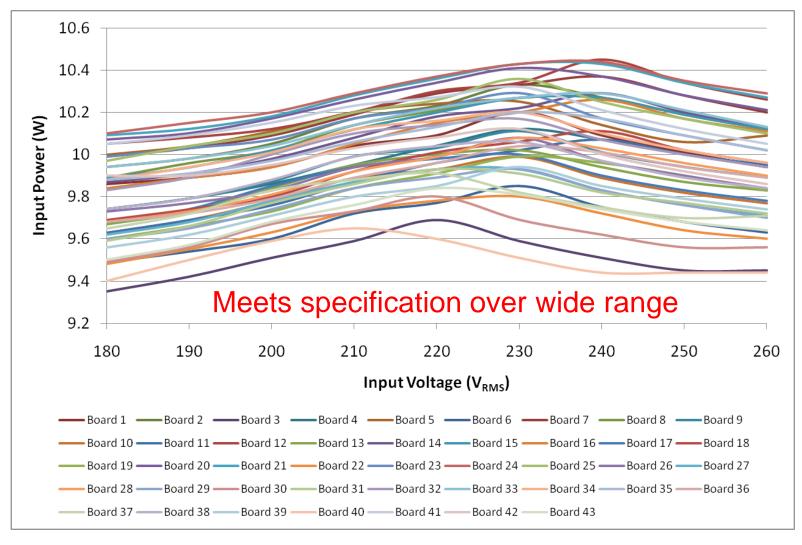Input Power vs. Input Voltage: Extended Range (180V to 260V)





LED Current vs. Input Voltage

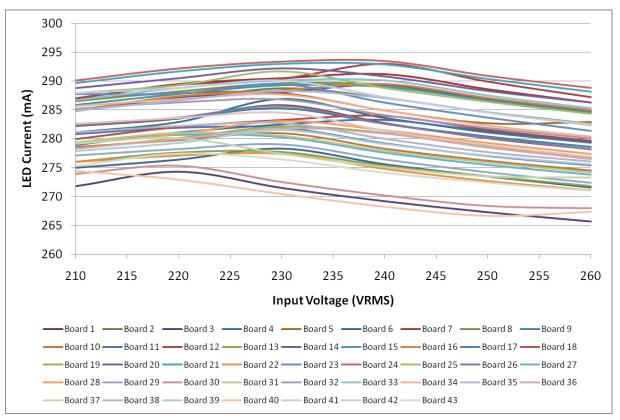


- LED current range for sample size of 43 boards ($210V_{RMS}$ to $260V_{RMS}$)
 - Min = 265.7mA(-5.74%)
 - Max = 293.5mA (+4.12%)
 - Average = 282mA

LED current deviation at any given voltage < ±7% (3 sigma)




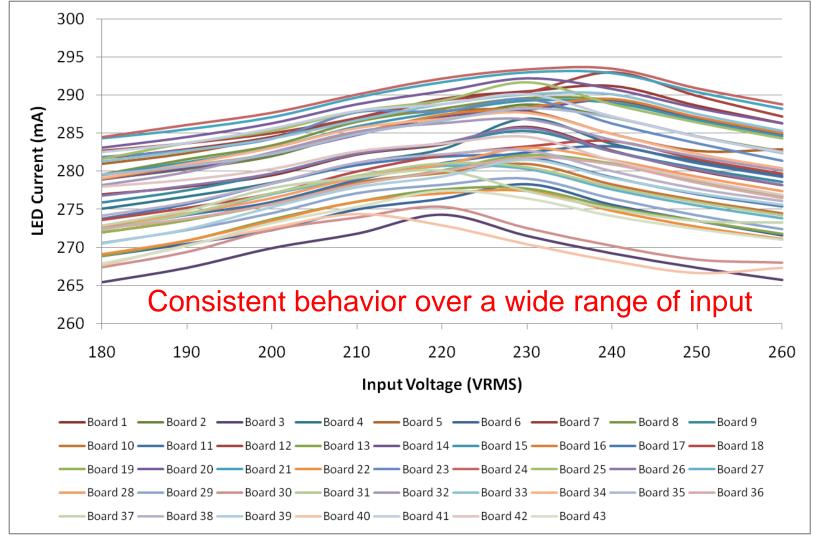LED Current vs. Input Voltage: Extended Range (180V to 260V)





Power Factor vs. Input Voltage

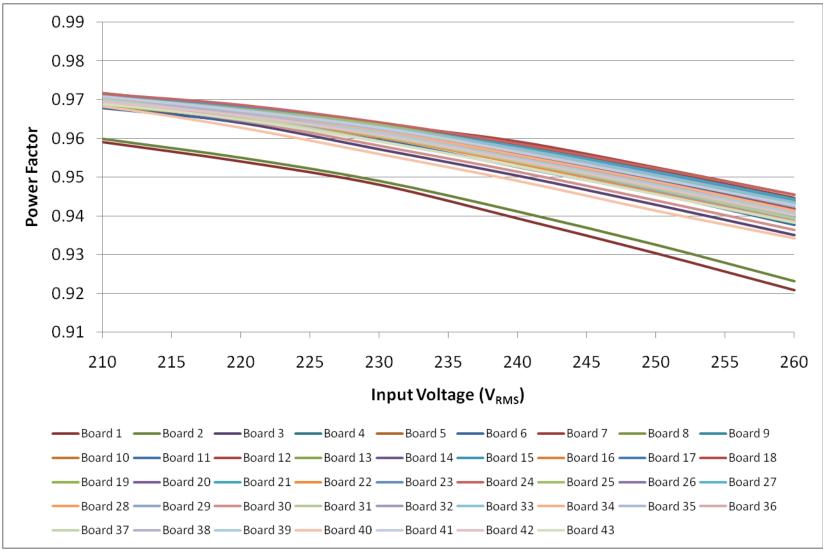




Summary


- Input power and LED current dependent on
 - Magnetizing inductance (L_M)
 - External resistors (R_{AC}, R_{FF})
 - Internal IC parameters $(G_{FF}, V_{REF}, f_S)^*$
- Theoretical analysis can be performed based on mathematical relation derived DCM Flyback PFC converter
- Experimental analysis performed for LM3447-A19-230VEVM using a sample size of 43 boards and 10 series connected Luxeon Rebel LED load board
 - Input power variation at $230V_{RMS}$, $50Hz = \pm 6.6\%$ (3 sigma)
 - LED current variation at $230V_{RMS}$, $50Hz = \pm 6.19\%$ (3 sigma)
 - Input power variation at any voltage between 210-260V < ±7.5% (3 sigma)
 - LED current variation at any voltage between $210-260V < \pm 7\%$ (3 sigma)
- Input power variation is within the desired specification over input range (3 sigma)
- LED current variation is close to the desired specification over input range (3 sigma)
- Expecting lower luminous flux variation over different LED bins, operating temperature and life time using power regulation approach
- Improved LED current matching can be achieved by reducing magnetizing inductance variation during manufacturing

* Contact TI for more information TI Information – Selective Disclosure



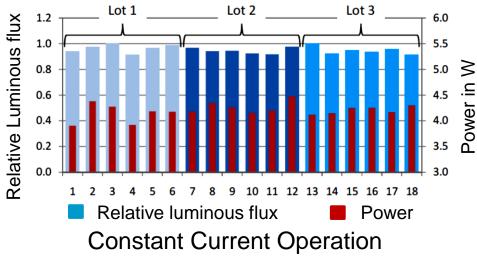Discussion: Comparing Power Regulation with Current Regulation Control



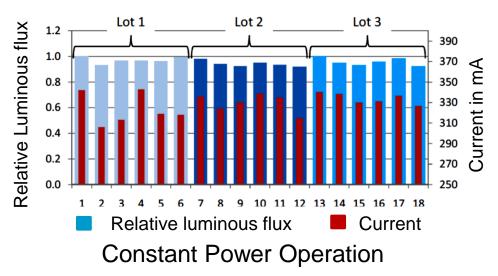

- Measured experimental data for 18 CREE MC-E LEDs
- Constant current (350 mA) operation
 - Maximum luminous flux difference of 8.5%
- Constant power (4 W) operation
 - Maximum luminous flux difference of 6.7%
- Power regulation approach is suggested to be better than current regulation when considering LED manufacturing variations



Delivering MORE Together

