

## **CC11xx Sensitivity versus Frequency Offset and Crystal Accuracy**

By Sverre Hellan

---

### **Keywords**

- *Sensitivity*
- *Frequency Offset*
- *Crystal Accuracy*
- *PER (Packet Error Rate)*
- *CC1100*
- *CC1100E*
- *CC1101*
- *CC1110*
- *CC1111*
- *CC430*

### **1 Introduction**

This design note provides plots of CC11xx (CC1100, CC1100E, CC1101, CC1110, and CC1111) sensitivity versus frequency offset for different data rates. The required

crystal accuracy is calculated from these plots. The results are also applicable for CC430.

## Table of Contents

KEYWORDS.....	1
1 INTRODUCTION.....	1
2 ABBREVIATIONS.....	2
3 RECEIVER CHANNEL FILTER BANDWIDTH AND CRYSTAL INACCURACIES .....	3
4 PER VERSUS FREQUENCY OFFSET .....	4
5 CRYSTAL ACCURACY.....	5
APPENDIX A: SENSITIVITY VERSUS FREQUENCY OFFSET .....	6
5.1 4.8 KBPS .....	6
5.2 10 KBPS .....	7
5.3 38.4 KBPS .....	8
5.4 250 KBPS .....	9
5.5 500 KBPS .....	10
6 GENERAL INFORMATION .....	11
6.1 DOCUMENT HISTORY.....	11

## 2 Abbreviations

FSK	Frequency Shift Keying
IF	Intermediate Frequency
MSK	Minimum Shift Keying
PER	Packet Error Rate
PLL	Phase Locked Loop
ppm	parts per million
SoC	System-on-Chip

## 3 Receiver Channel Filter Bandwidth and Crystal Inaccuracies

A phase locked loop (PLL) is used to generate the RF frequency in the CC1100/CC1101/CC1100E transceiver and CC1110/CC1111/CC430 SoC. The PLL reference frequency is derived from an external crystal. If the crystal frequency is incorrect, the transmitter carrier frequency and the receiver LO frequency will also be incorrect. The crystal frequency error is due to initial tolerance, capacitive loading errors, ageing, and temperature drift.

**Example:** If the crystal frequency has an error of  $\pm X$  ppm (parts per million) the RF frequency also has an error of  $\pm X$  ppm. As an example, if the crystal error is +10 ppm and the CC11xx is programmed for a carrier frequency of 868 MHz, there will be an error in the carrier frequency of  $868 \text{ MHz} \cdot 10/10^6 = 8.68 \text{ kHz}$ .

The transmitted signal will have a certain signal bandwidth ( $BW_{\text{signal}}$ ), which depends on the data rate and modulation format. On the receiver side there is a channel filter, which is centered on the down-converted received RF frequency, i.e. the intermediate frequency (IF). The channel filter has a programmable bandwidth  $BW_{\text{channel}}$ . The signal bandwidth has to be less than the receiver channel filter bandwidth, but we also have to take the frequency error of the transmitter and receiver into account.

If there is an error in the transmitter carrier frequency and the receiver LO frequency, there will also be an error in the IF frequency. For simplicity assume the frequency error in the transmitter and receiver is equal (same type of crystal). If the receiver has an error of  $-X$  ppm and the transmitter has an error of  $+X$  ppm the IF frequency will have an error of  $+2 \cdot X$  ppm (CC11xx uses low side LO injection). Conversely, if the receiver has an error of  $+X$  ppm and the transmitter an error of  $-X$  ppm the IF frequency will have an error of  $-2 \cdot X$  ppm.

**Example:** If the transmitter crystal error is +10 ppm and the CC11xx is programmed for a carrier frequency of 868 MHz, there will be an error in the carrier frequency of 8.68 kHz. If the receiver crystal error is -10 ppm and the CC11xx is programmed for an LO frequency of 867.7 MHz (300 kHz IF frequency) there will be an error in the LO frequency of -8.677 kHz (approximately the same as the error in the carrier frequency due to the low IF frequency used). The total error in the IF frequency, after down conversion from RF, will be  $2 \cdot 8.68 \text{ kHz} = 17.4 \text{ kHz}$ .

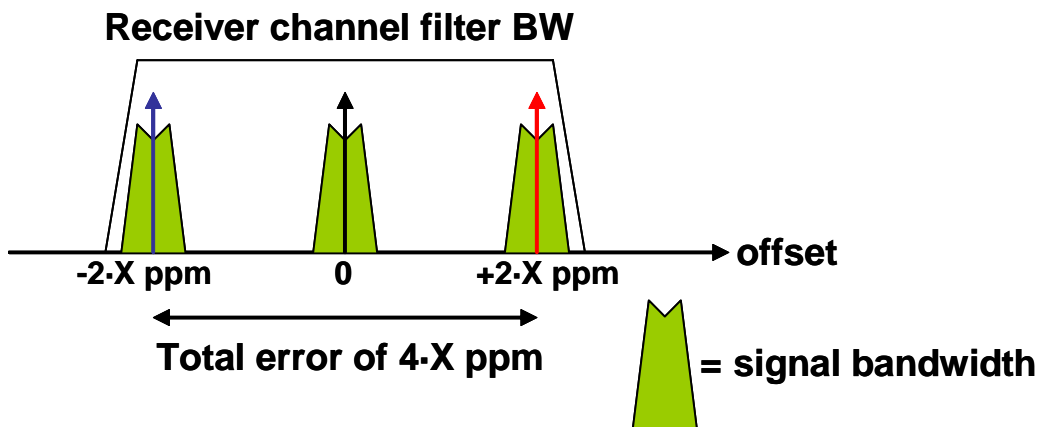


Figure 1. Plot of IF versus frequency error

Figure 1 shows the required minimum channel filter bandwidth  $BW_{\text{channel}}$  to account for crystal errors of opposite signs, which is a worst case scenario.  $BW_{\text{channel}}$  has to be larger than the maximum signal bandwidth  $BW_{\text{signal}}$  plus the maximum frequency error due to crystal inaccuracies.

$$BW_{\text{channel}} > BW_{\text{signal}} + 4 \cdot XTAL_{\text{ppm}} \cdot f_{\text{RF}}$$

where


- $XTAL_{ppm}$  is the total accuracy of the crystal including initial tolerance, temperature drift, loading, and ageing
- $f_{RF}$  is the RF operating frequency.

Example: If both the transmitter and receiver crystal accuracy is  $\pm 10$  ppm and the CC11xx is programmed for a carrier frequency of 868 MHz with an IF frequency of 300 kHz,  $BW_{channel}$  must be larger than  $BW_{signal} + 4 \cdot XTAL_{ppm} \cdot f_{RF} = BW_{signal} + 4 \cdot 8.68$  kHz.


## 4 PER versus Frequency Offset

Figure 6 to Figure 12 plots the 1% PER for different data rates and modulation formats. Register FOCCFG.FOC\_LIMIT[1:0] = 11<sub>b</sub> and the RF frequency is 868 MHz in the measurements. Since the signal bandwidth is given, the plots can be used to estimate the maximum frequency offset and hence the required crystal accuracy.

Assuming a 3 dB loss in sensitivity is acceptable, the *total* frequency offset is estimated as 2 times the frequency offset where a 3 dB degradation in PER is first measured (see Figure 2). In the ideal case the 3 dB degradation in PER should occur at the same positive and negative frequency offsets (see Figure 3). Since the IF frequency is programmed in steps of 25 kHz this is not always possible.

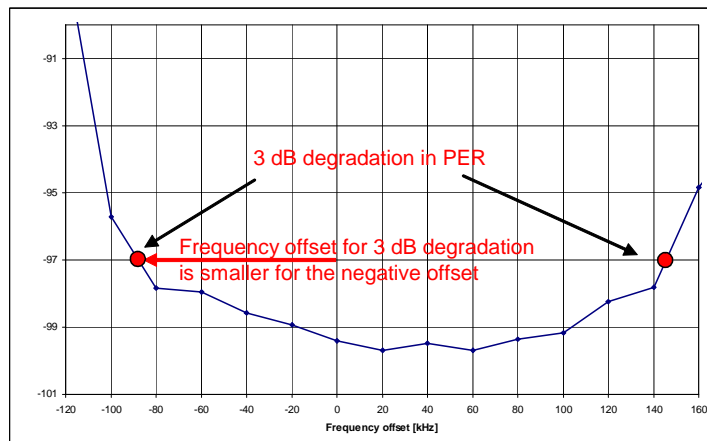

**Figure 2. Definition of frequency offset which gives 3 dB degradation on PER (unsymmetrical frequency offset)**

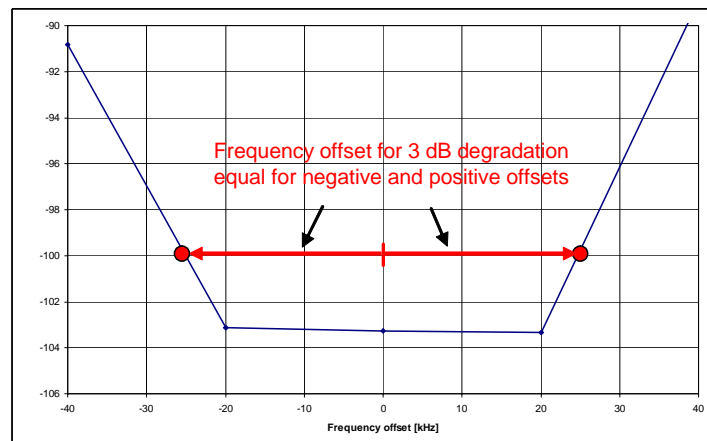

**Figure 3. Definition of frequency offset which gives 3 dB degradation on PER (symmetrical frequency offset)**

## 5 Crystal Accuracy

Appendix A shows plots of sensitivity versus frequency offset for different data rates. The required crystal accuracy is calculated from the total frequency offset as

$$\text{Total frequency offset} = 4 \cdot \text{XTAL}_{\text{ppm}} \cdot f_{\text{RF}}$$

$$\Rightarrow \text{Crystal accuracy (in ppm)} = \text{Total frequency offset} \cdot 1E^6 / (4 \cdot f_{\text{RF}})$$

Case	Figure	3 dB bandwidth (total frequency offset)	Crystal accuracy (@868 MHz)
4.8 kbps, 2FSK, 25 kHz deviation, DC filter. RX filter bandwidth = 101 kHz	Figure 4	50 kHz	±14 ppm
4.8 kbps, 2FSK, 25 kHz deviation, no DC filter. RX filter bandwidth = 101 kHz	Figure 5	50 kHz	±14 ppm
10 kbps, 2FSK, 19 kHz deviation, DC filter. RX filter bandwidth = 101 kHz	Figure 6	70 kHz	±20 ppm
10 kbps, 2FSK, 19 kHz deviation, no DC filter. RX filter bandwidth = 101 kHz	Figure 7	70 kHz	±20 ppm
38.4 kbps, 2FSK, 20 kHz deviation, DC filter. RX filter bandwidth = 101 kHz	Figure 8	110 kHz	±32 ppm
38.4 kbps, 2FSK, 20 kHz deviation, no DC filter. RX filter bandwidth = 101 kHz	Figure 9	120 kHz	±35 ppm
76.8 kbps, 2FSK, 32 kHz deviation, DC filter. RX filter bandwidth = 232 kHz	-	230 kHz	±66 ppm
76.8 kbps, 2FSK, 32 kHz deviation, no DC filter. RX filter bandwidth = 232 kHz	-	260 kHz	±75 ppm
100 kbps, 2FSK, 47 kHz deviation, DC filter. RX filter bandwidth = 325 kHz	-	220 kHz	±63 ppm
100 kbps, 2FSK, 47 kHz deviation, no DC filter. RX filter bandwidth = 325 kHz	-	180 kHz	±52 ppm
250 kbps, MSK, DC filter. RX filter bandwidth = 541 kHz	Figure 10	200 kHz	±58 ppm
250 kbps, MSK, no DC filter. RX filter bandwidth = 541 kHz	Figure 11	220 kHz	±63 ppm
500 kbps, MSK, DC filter. RX filter bandwidth = 812 kHz	Figure 12	120 kHz	±35 ppm

**Table 1: Crystal Accuracy Requirement for Selected Data Rates and Modulation Formats with FOCCFG.FOC\_LIMIT[1:0] = 11<sub>b</sub>**

Note: The ADC spectrum in the RX chain consists of a significant DC component. This puts a lower limit on the IF frequency that can be used. For optimum sensitivity, a digital DC filter can be enabled (MDMCFG2.DEM\_DCFILT\_OFF = 0), and the ADC DC output is attenuated. This opens for selection of lower IF frequencies thereby lower noise floor and improved

sensitivity. As an example, for 868 MHz, 250 kbps 2-FSK, enabling the DC filter gives 2 dB better sensitivity, at the expense of an increased current consumption of 2.3 mA

## Appendix A: Sensitivity versus frequency offset

### 5.1 4.8 kbps

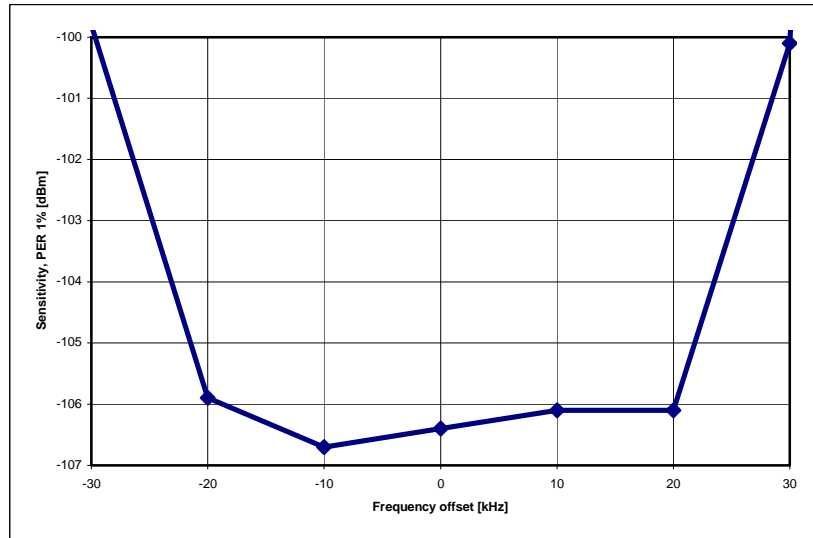


Figure 4. 4.8 kbps, MDMCFG2.DEM\_DCFLT\_OFF = 0

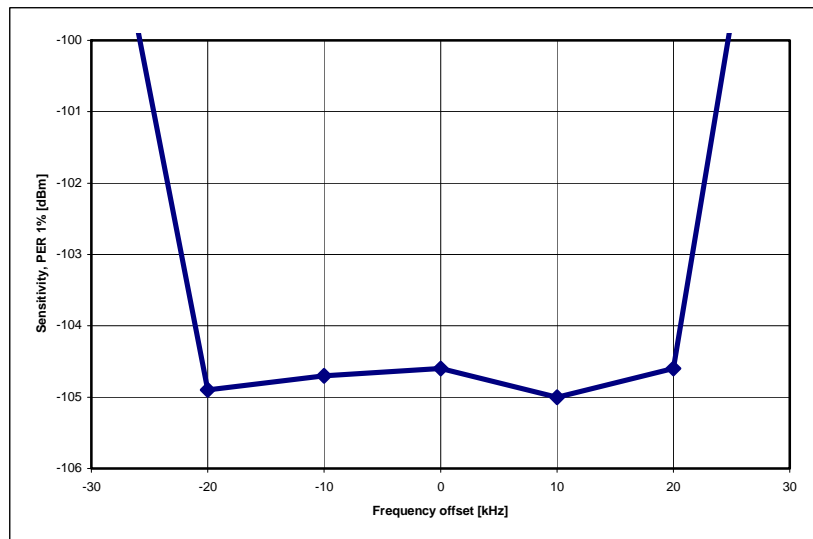


Figure 5. 4.8 kbps, MDMCFG2.DEM\_DCFLT\_OFF = 1

## 5.2 10 kbps

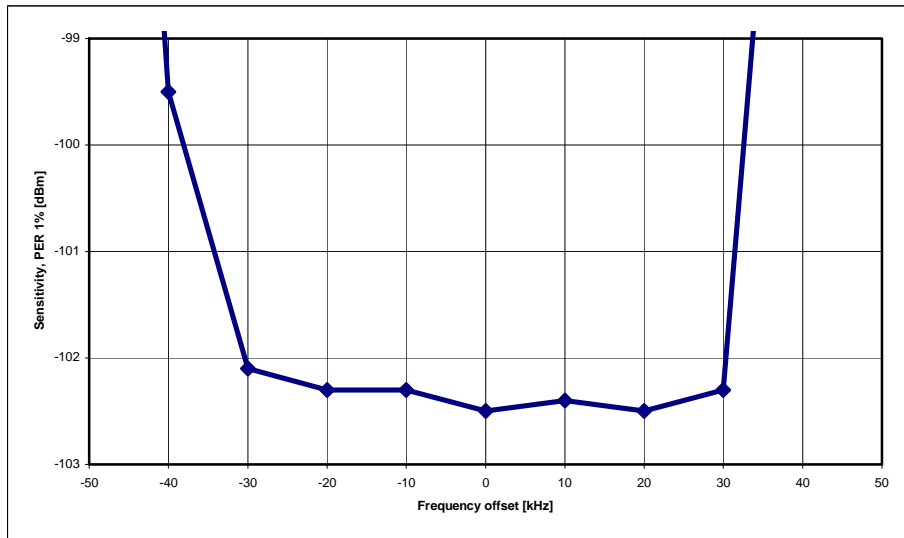


Figure 6. 10 kbps, MDMCFG2.DEM\_DCFILT\_OFF = 0

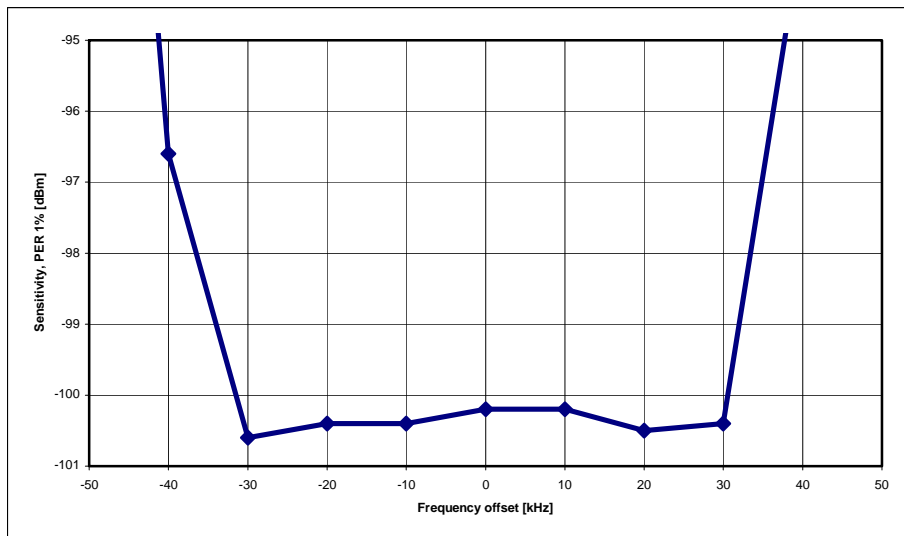


Figure 7. 10 kbps, MDMCFG2.DEM\_DCFILT\_OFF = 1

## 5.3 38.4 kbps

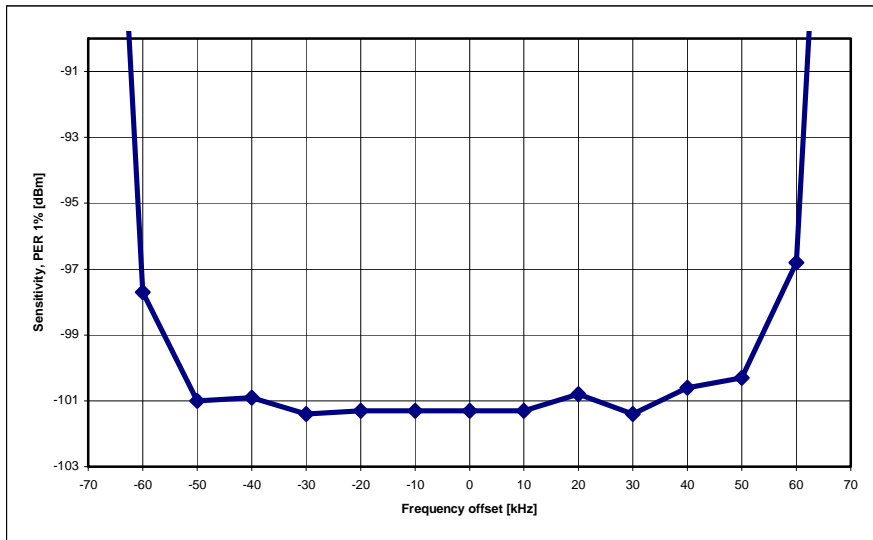


Figure 8. 38.4 kbps, MDMCFG2.DEM\_DCFILT\_OFF = 0

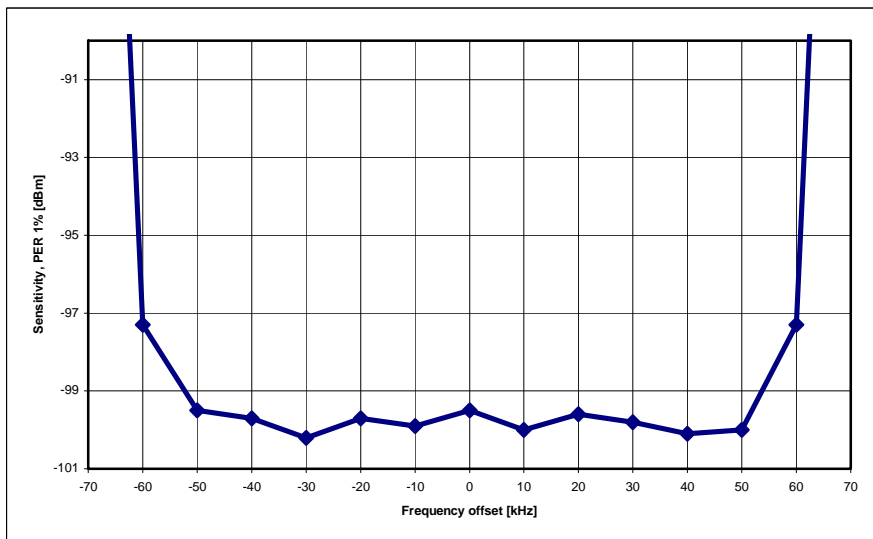


Figure 9. 38.4 kbps, MDMCFG2.DEM\_DCFILT\_OFF = 1



## 5.4 250 kbps

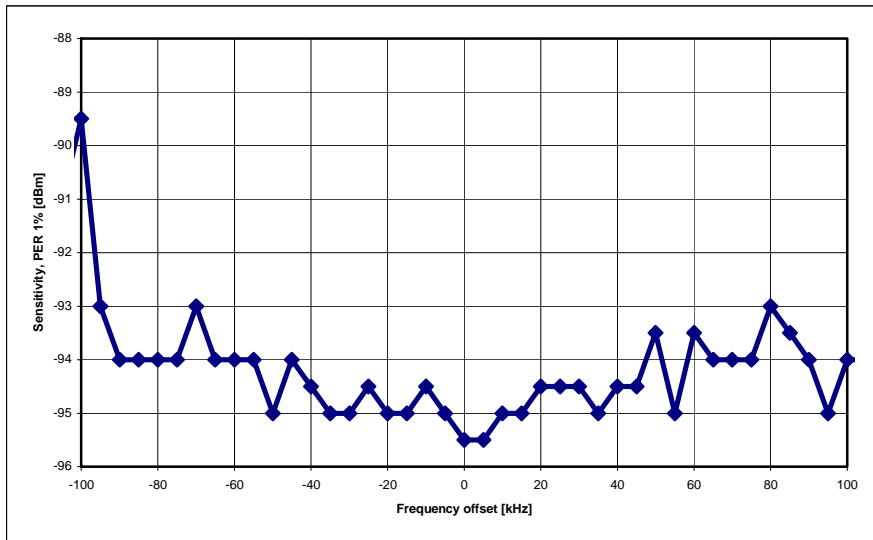


Figure 10. 250 kbps, MDMCFG2.DEM\_DCFILT\_OFF = 0

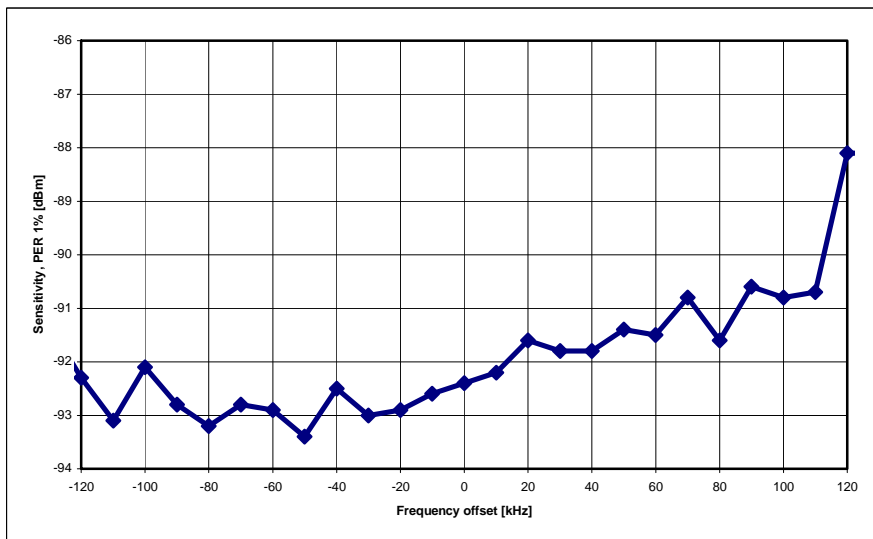


Figure 11. 250 kbps, MDMCFG2.DEM\_DCFILT\_OFF = 1

5.5 500 kbps

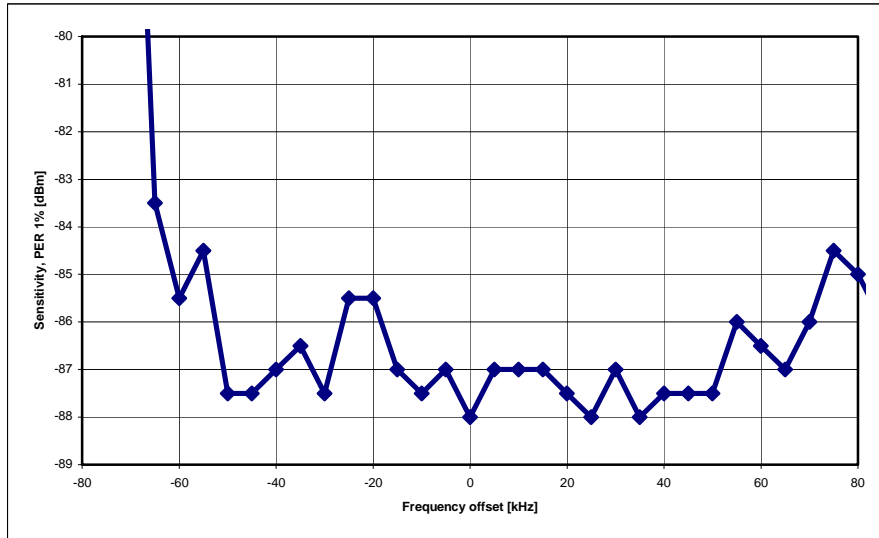


Figure 12. 500 kbps, MDMCFG2.DEM\_DECFILT\_OFF = 0

## 6 General Information

### 6.1 Document History

Revision	Date	Description/Changes
SWRA122C	2009.08.20	Added CC430
SWRA122B	2009.03.13	Added CC1100E
SWRA122A	2007.12.17	Added CC1101 and CC1111 Removed logo from header
SWRA122	2006.11.27	Initial release

## IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

### Products

Amplifiers	<a href="http://amplifier.ti.com">amplifier.ti.com</a>
Data Converters	<a href="http://dataconverter.ti.com">dataconverter.ti.com</a>
DLP® Products	<a href="http://www.dlp.com">www.dlp.com</a>
DSP	<a href="http://dsp.ti.com">dsp.ti.com</a>
Clocks and Timers	<a href="http://www.ti.com/clocks">www.ti.com/clocks</a>
Interface	<a href="http://interface.ti.com">interface.ti.com</a>
Logic	<a href="http://logic.ti.com">logic.ti.com</a>
Power Mgmt	<a href="http://power.ti.com">power.ti.com</a>
Microcontrollers	<a href="http://microcontroller.ti.com">microcontroller.ti.com</a>
RFID	<a href="http://www.ti-rfid.com">www.ti-rfid.com</a>
RF/IF and ZigBee® Solutions	<a href="http://www.ti.com/lprf">www.ti.com/lprf</a>

### Applications

Audio	<a href="http://www.ti.com/audio">www.ti.com/audio</a>
Automotive	<a href="http://www.ti.com/automotive">www.ti.com/automotive</a>
Broadband	<a href="http://www.ti.com/broadband">www.ti.com/broadband</a>
Digital Control	<a href="http://www.ti.com/digitalcontrol">www.ti.com/digitalcontrol</a>
Medical	<a href="http://www.ti.com/medical">www.ti.com/medical</a>
Military	<a href="http://www.ti.com/military">www.ti.com/military</a>
Optical Networking	<a href="http://www.ti.com/opticalnetwork">www.ti.com/opticalnetwork</a>
Security	<a href="http://www.ti.com/security">www.ti.com/security</a>
Telephony	<a href="http://www.ti.com/telephony">www.ti.com/telephony</a>
Video & Imaging	<a href="http://www.ti.com/video">www.ti.com/video</a>
Wireless	<a href="http://www.ti.com/wireless">www.ti.com/wireless</a>

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2009, Texas Instruments Incorporated